

Problem 5.1:

$$Q = C \Delta V$$

← Voltage ← { 3.3 → 12VDC is common


↑ "Stored" charge

↑ capacitance proportionality w/ Voltage

Larger capacitor will store more charge @ the same voltage.

$$\Delta V = \frac{Q}{C}$$
$$= \frac{3.1 \text{ E-6}}{2 \text{ E-6}} = \boxed{1.55 \text{ V}}$$

Problem 5.2:

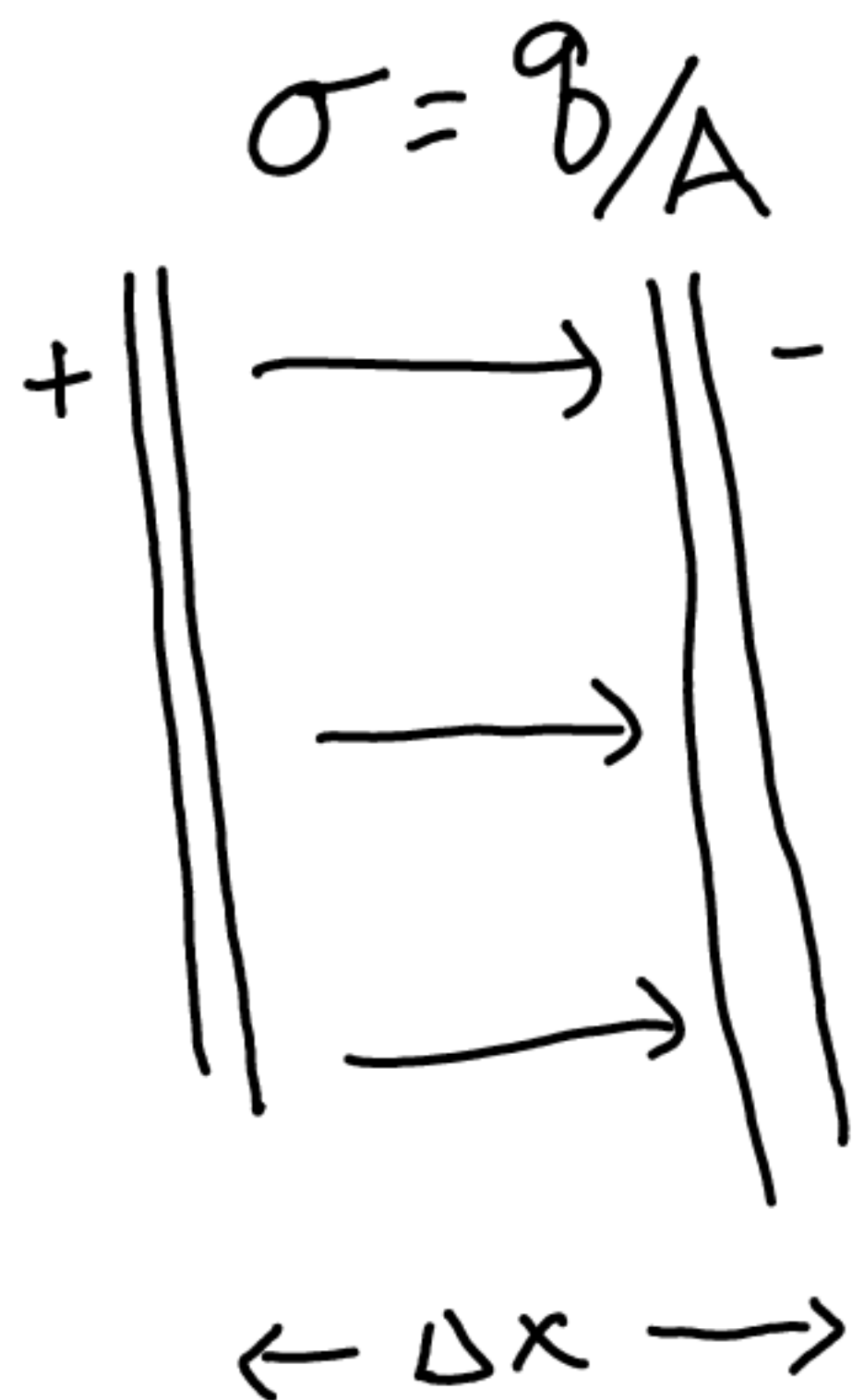

$\Delta V = \int \vec{E} \cdot d\vec{l} \Rightarrow E \Delta x$ w/ constant \vec{E}

→ $\Delta V = \frac{\sigma}{\epsilon_0} \Delta x$

$\vec{E} = \frac{\sigma}{\epsilon_0} \hat{x}$

$$\Delta V = \frac{Q}{\epsilon_0 A} \Delta x$$


$$Q = \left(\frac{\epsilon_0 A}{\Delta x} \right) \Delta V$$

↑ capacitance

$$C = \frac{\epsilon_0 A}{\Delta x}$$

$$A = \frac{C \Delta x}{\epsilon_0} = \frac{(5 \text{ E-9})(0.002)}{(8.85 \text{ E-12})} = \boxed{1.3 \text{ m}^2}$$

plane

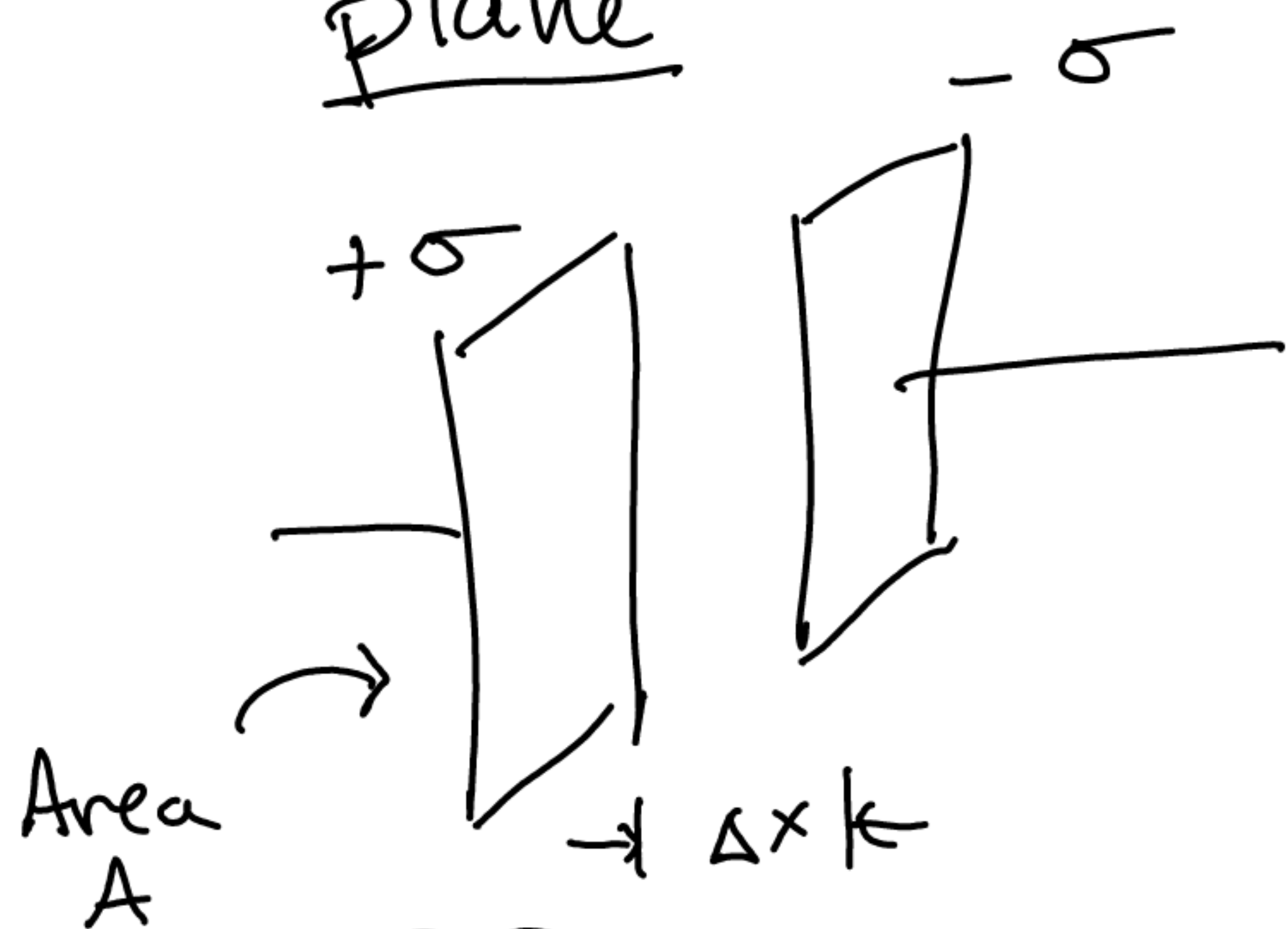

set charge as $q = \sigma A$
Evaluate $\vec{E} \cdot d\vec{l} \Rightarrow$ Voltage.

$$-\int E \cdot dl = -E \int dx = -E \Delta x = \Delta V$$

Gauss

$$E(2A) = \frac{\sigma A}{\epsilon_0}$$

$$E = \sigma / 2\epsilon_0 \Rightarrow E = \frac{\sigma}{\epsilon_0}$$


$$Q = C \Delta V =$$

$$\sigma A = C(E \Delta x) = C\left(\frac{\sigma}{\epsilon_0} \Delta x\right)$$

$$C = \frac{\epsilon_0 A}{\Delta x}$$

plane of charge

cylinder

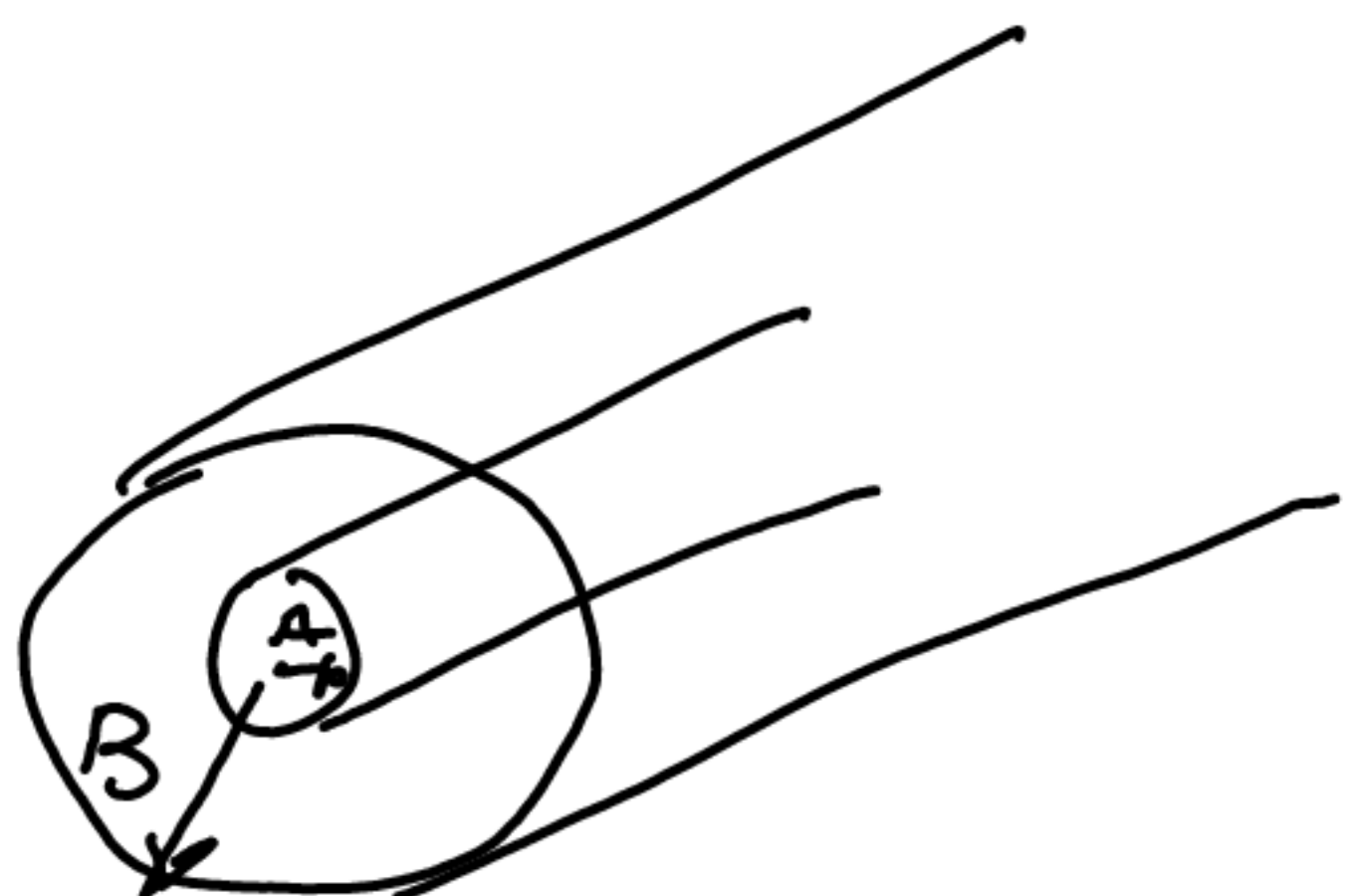

$$q = \lambda l$$

$$\Delta V = -\int \vec{E} \cdot d\vec{l} = \int \frac{\lambda}{2\pi\epsilon_0 r} \hat{r} \cdot dr \hat{r}$$

$$= -\frac{\lambda}{2\pi\epsilon_0} \int \frac{dr}{r} = \frac{\lambda}{2\pi\epsilon_0} \ln(r) \Big|_A^B$$

$$Q = C \Delta V = C \left[\frac{Q}{l} \frac{1}{2\pi\epsilon_0} \ln\left(\frac{A}{B}\right) \right]$$


Gauss

$$E(2\pi r l) = \frac{\lambda l}{\epsilon_0}$$

$$\vec{E} = \frac{\lambda}{2\pi\epsilon_0 r} \hat{r}$$

$$C = 2\pi\epsilon_0 l \ln\left(\frac{A}{B}\right)$$

Sphere:

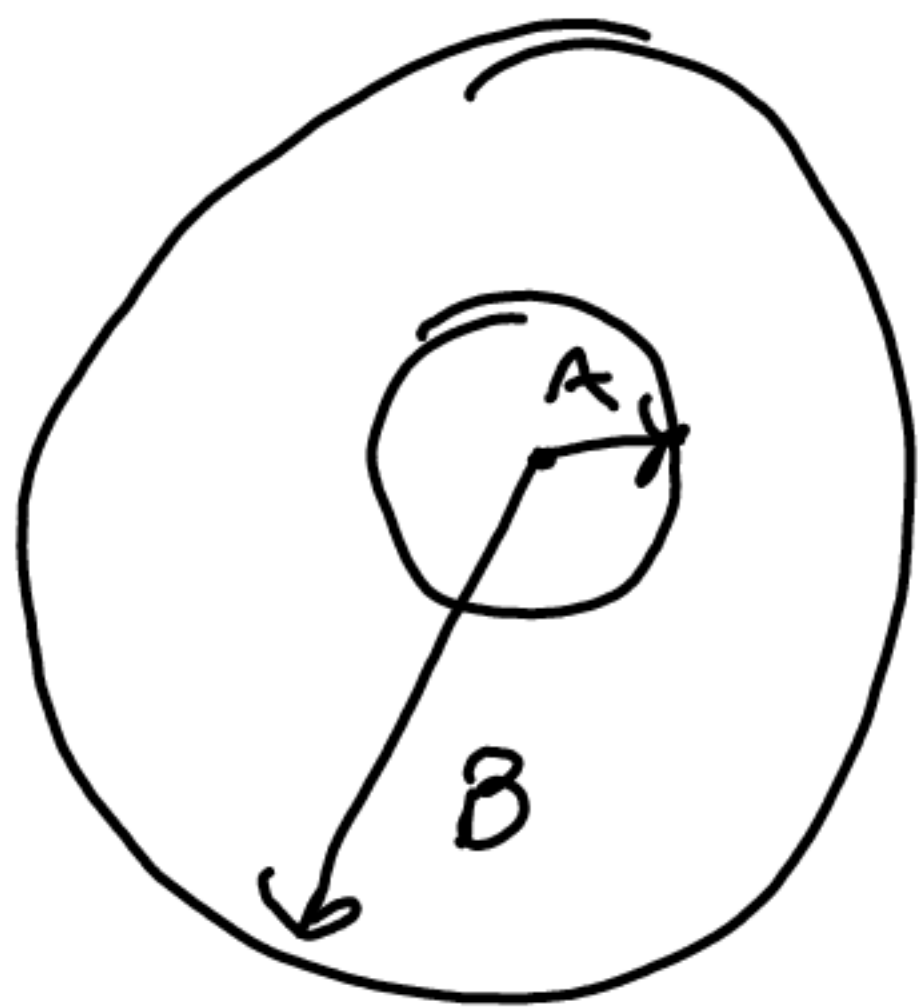

Gauss:

$$E(4\pi r^2) = \frac{Q}{\epsilon_0}$$

$$E = \frac{Q}{4\pi\epsilon_0 r^2} \hat{r}$$

$$\Delta V = - \int \vec{E} \cdot d\vec{l}$$

$$= - \int \frac{Q}{4\pi\epsilon_0 r^2} \hat{r} \cdot dr \hat{r}$$

$$= - \frac{Q}{4\pi\epsilon_0 r} \Big|_A^B = \frac{Q}{4\pi\epsilon_0} \left[\frac{1}{A} - \frac{1}{B} \right]$$

$$Q = C \Delta V$$

$$Q = C \left[\frac{Q}{4\pi\epsilon_0} \left(\frac{1}{A} - \frac{1}{B} \right) \right]$$

$$C = 4\pi\epsilon_0 \frac{1}{\frac{1}{A} - \frac{1}{B}}$$


to simplify: $\frac{1}{A} - \frac{1}{B} = \frac{B}{AB} - \frac{A}{AB}$

$$= \frac{B-A}{AB}$$

$$C = 4\pi\epsilon_0 \left(\frac{AB}{B-A} \right)$$

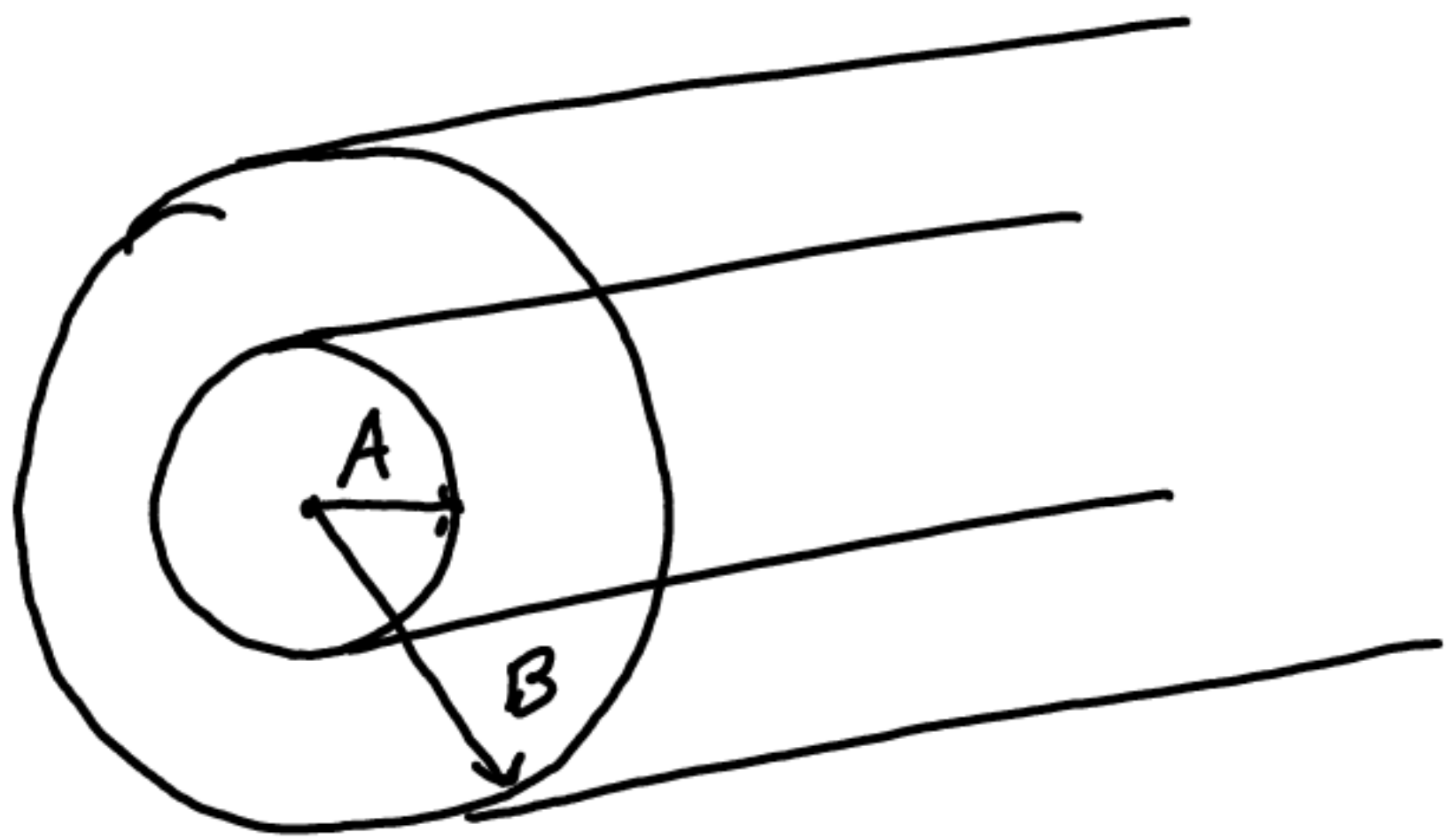Problem 5.3:

$$C = 2\pi\epsilon_0 l \ln\left(\frac{A}{B}\right)$$



$$\frac{C}{l} = 20 \text{E-12} \frac{\text{F}}{\text{m}}$$

milli - 3
micro - 6
nano - 9
pico - 12


$$\frac{C}{l} = 2\pi\epsilon_0 \ln\left(\frac{A}{B}\right)$$

ratio

$$\frac{A}{B} = \exp\left(\frac{C}{2\pi\epsilon_0 l}\right) = \exp\left(\frac{20\text{E-12}}{2\pi(8.85\text{E-12})}\right) = \boxed{1.43}$$

problem 5.4


"series" then "parallel" reduction

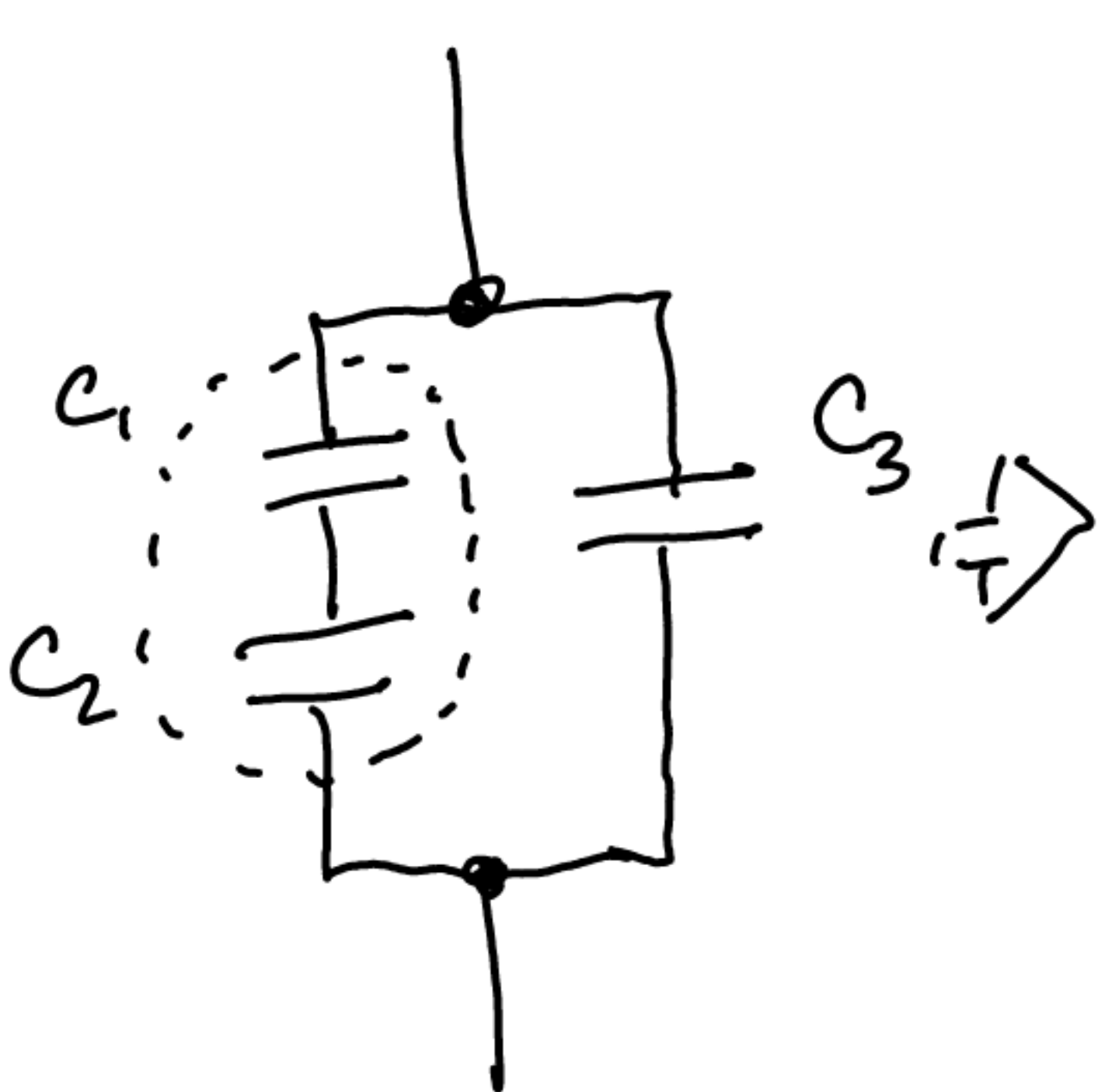

series

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

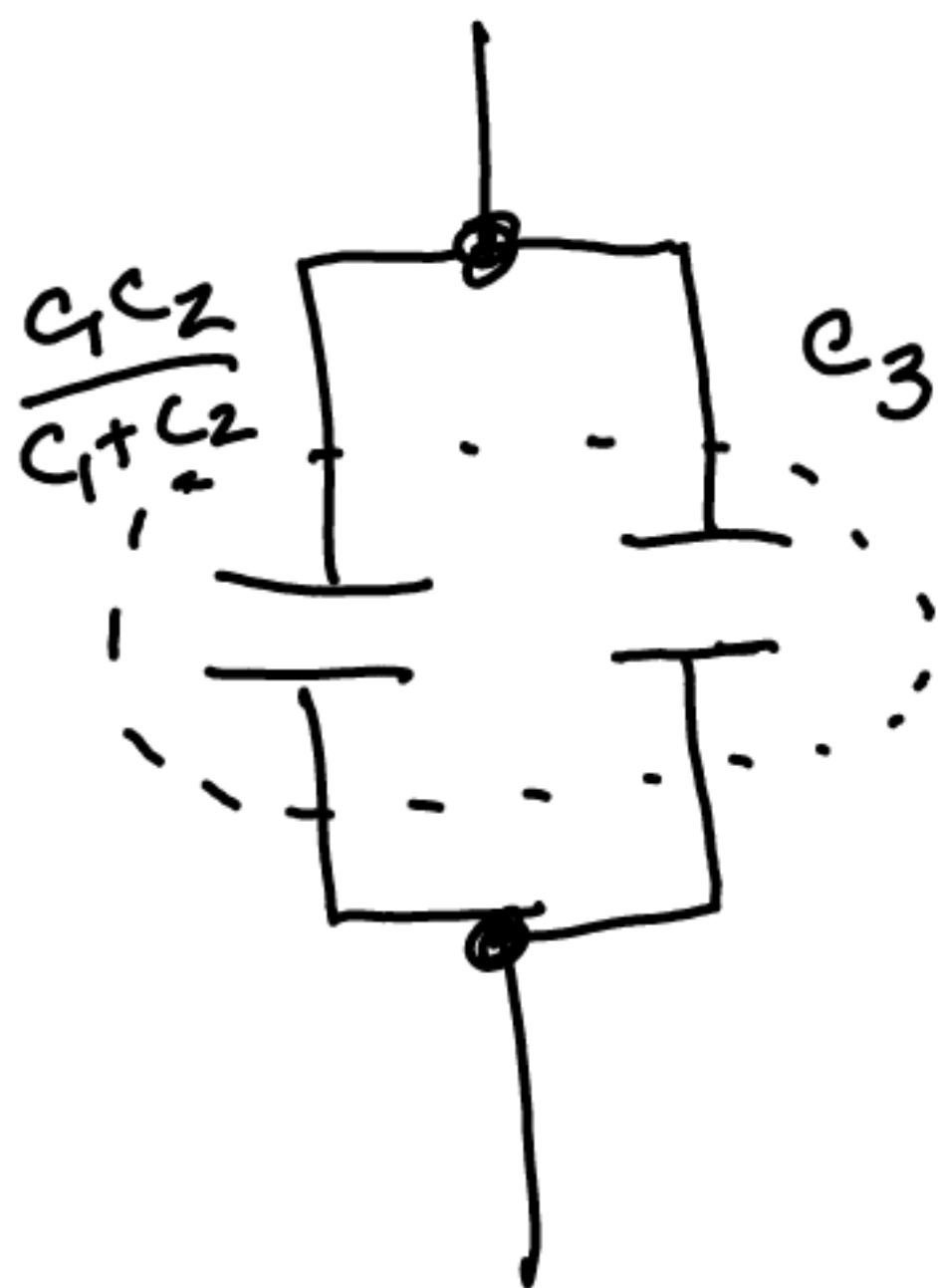


parallel

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} + C_3$$


$$= \boxed{2.79 \mu\text{F}}$$

problem 5.5

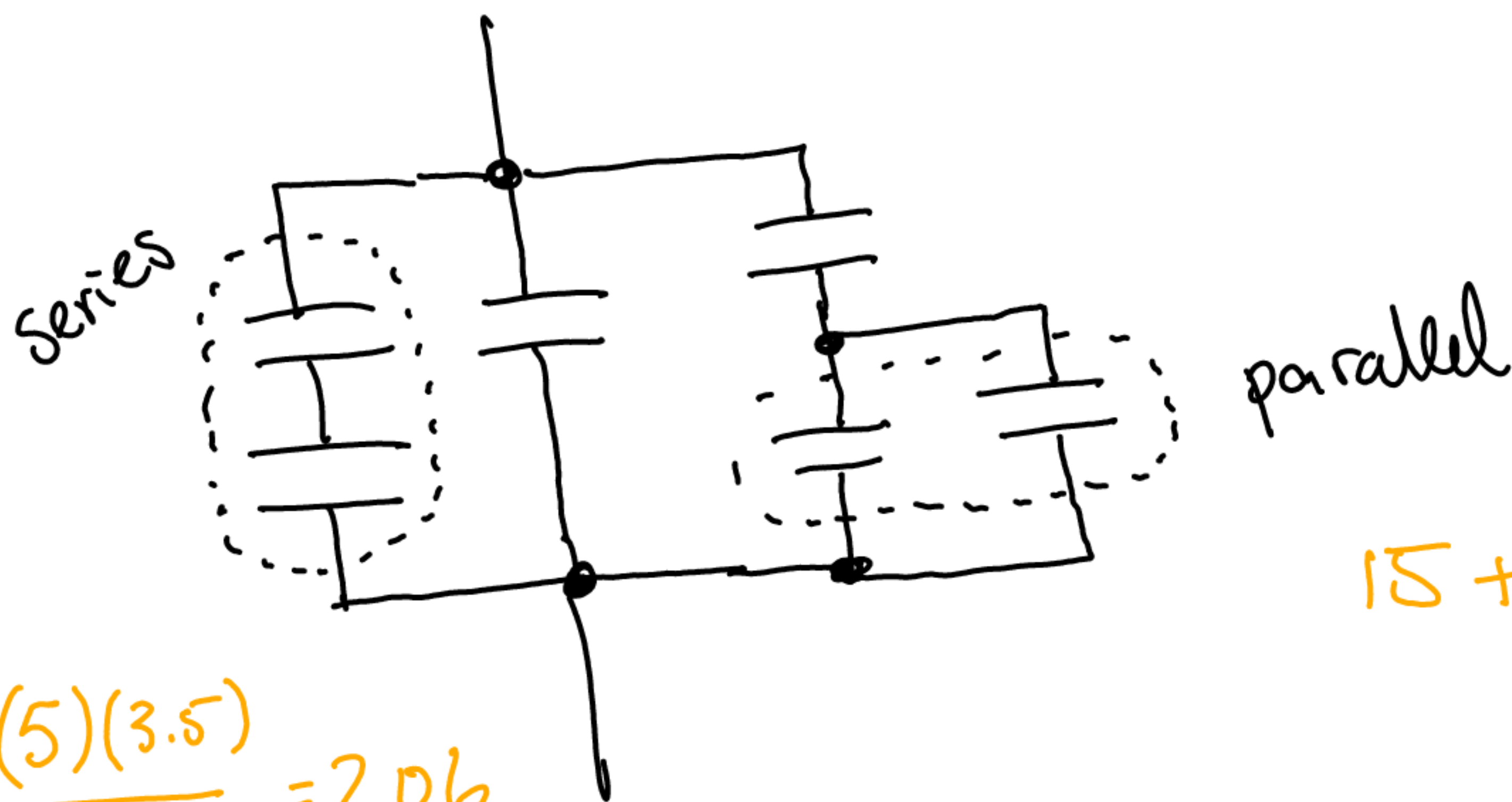


$$15 + 0.75 = 15.75$$

$$\frac{(5)(3.5)}{5 + 3.5} = 2.06$$

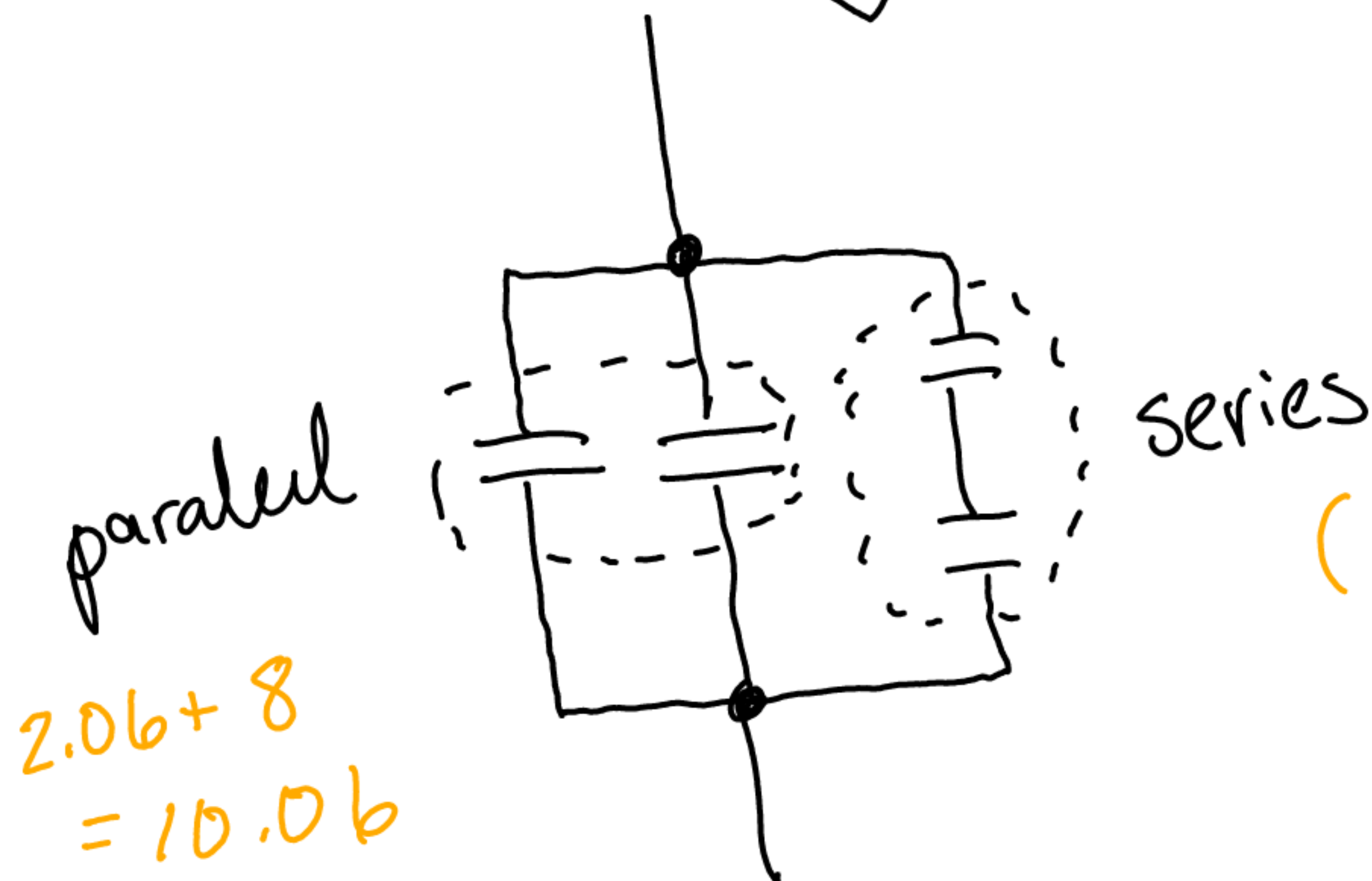

$$2.06 + 8 = 10.06$$
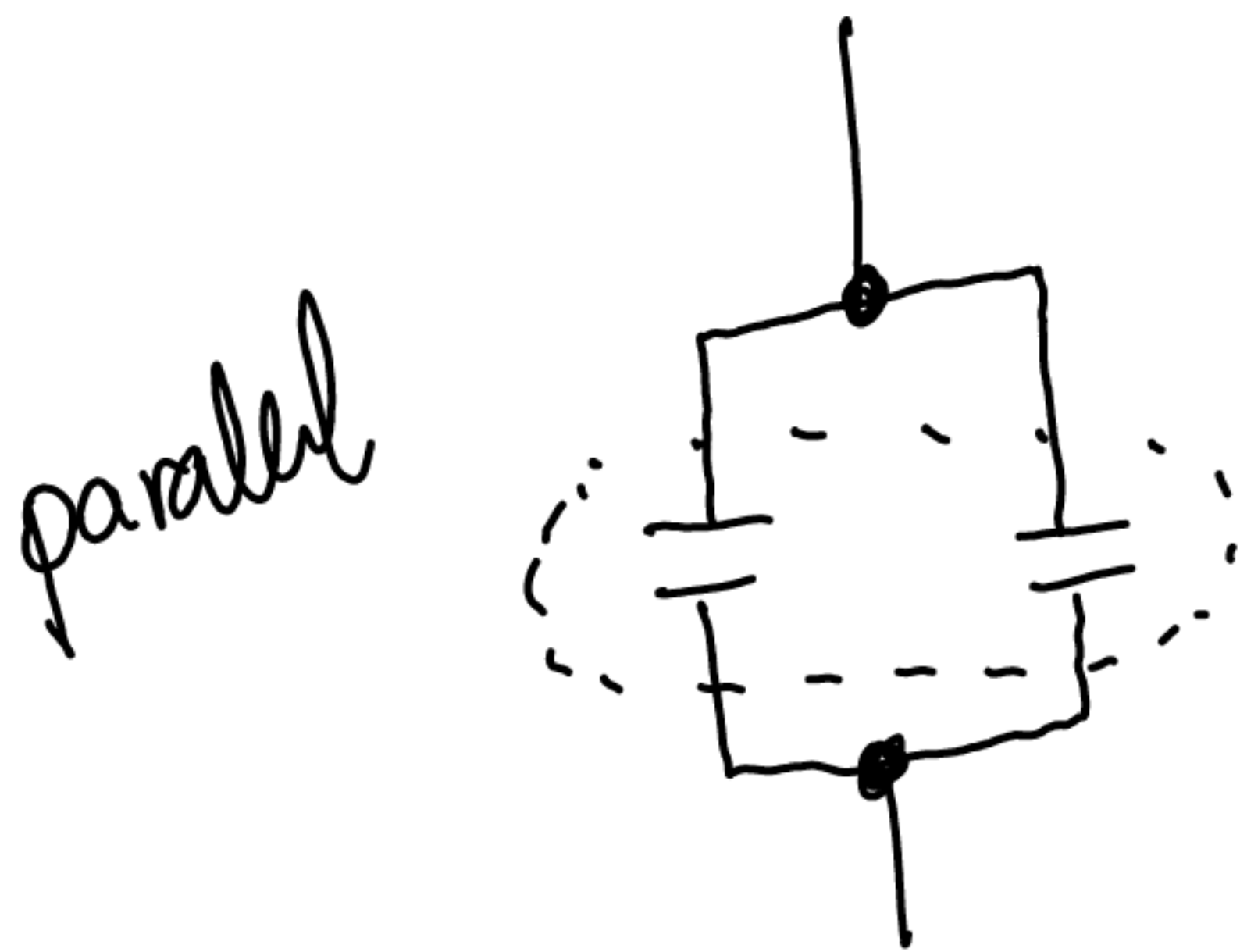
$$\frac{(1.5)(15.75)}{1.5 + 15.75} = 1.37$$




$$10.06 + 1.37$$



$$C_{eq} = 11.43 \mu F$$

Problem 5.6:


First charge the 40 pF cap at 500 Volts

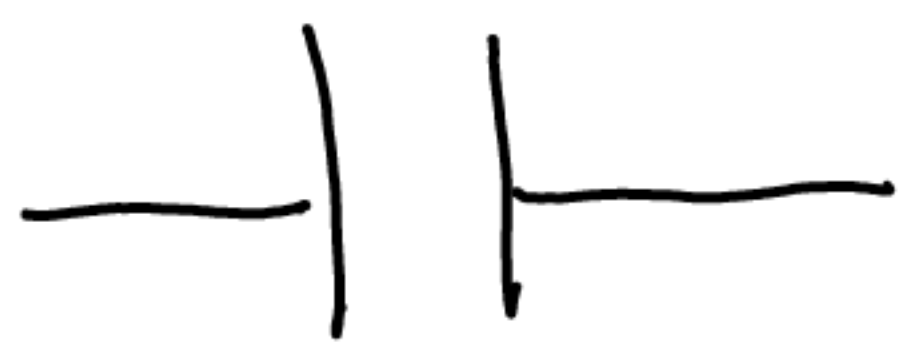

$$Q = C\Delta V = \boxed{20 \text{ nC}}$$

Then connect another cap: Two things remain true:

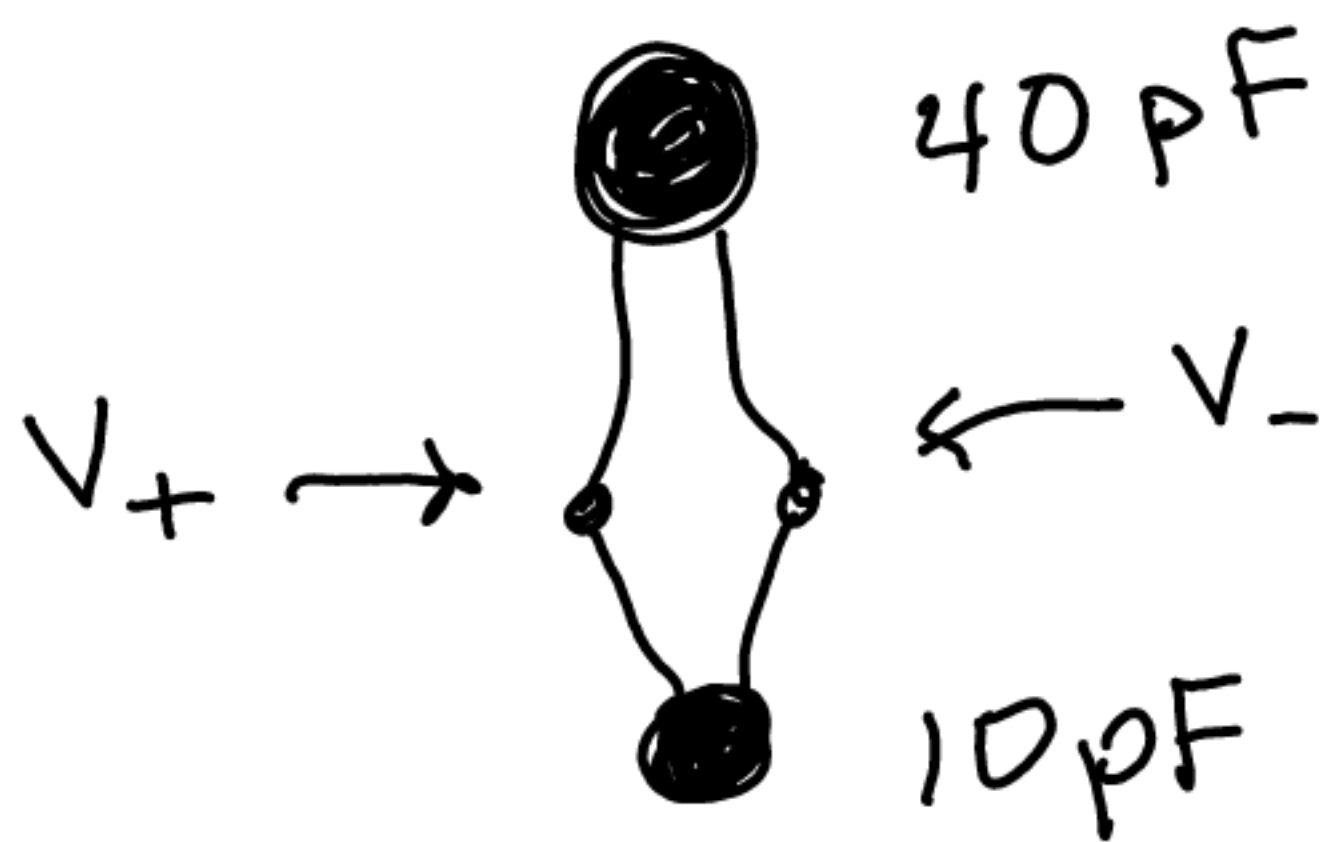- Charge is shared between both caps
↳ the electrons (or "lack of") can move along the wire, but charge cannot be destroyed.
- Voltage must be equal on each side
↳ the voltage drop on a wire is zero if as long as resistance is negligible $R=0$



$$Q = Q_1 + Q_2 = 20 \text{ nC}$$

$$\Delta V_1 = \Delta V_2$$

$$Q = Q_1 + Q_2 = C_1 \Delta V_1 + C_2 \Delta V_2 = (C_1 + C_2) \Delta V$$

$$\Delta V = \frac{Q}{C_1 + C_2} = \frac{20 \text{ nC}}{40 \text{ pF} + 10 \text{ pF}} = \boxed{400 \text{ V}}$$

problem 5.7

$$C = \frac{\epsilon_0 A}{\Delta x} \quad \text{parallel plate cap}$$


$$C = \frac{(8.85 \times 10^{-12})(0.08)}{0.001} = \boxed{647 \text{ nF}}$$

if filled w/ Dielectric:

$$\epsilon = 6 \epsilon_0$$

$$\boxed{C = 3.88 \mu\text{F}}$$

problem 5.8:

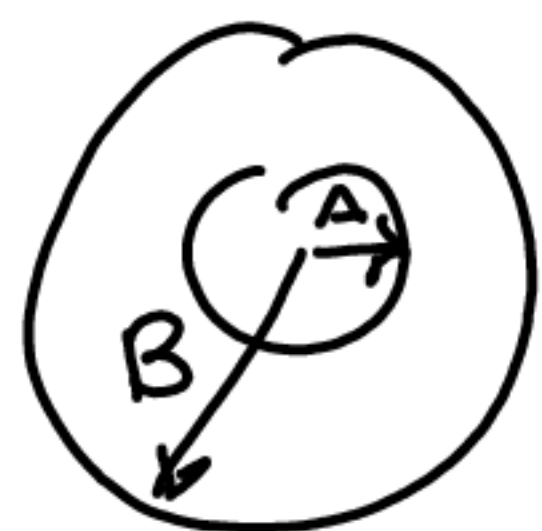

spherical capacitor

$$C = 4\pi\epsilon_0 \left[\frac{1}{\frac{1}{A} - \frac{1}{B}} \right]$$

$$A = 6.378 \times 10^6 \text{ m}$$

$$B = A + 70 \text{ km}$$

$$B = 6.448 \times 10^6 \text{ m}$$

$$C = 4\pi\epsilon_0 \frac{AB}{B-A}$$

$$C = 65.3 \text{ mF}$$

$$Q = C\Delta V = (65.3 \text{ E-3})(3.5 \text{ E5})$$

$$= 22.9 \text{ KiloCoulomb}$$

$$Q = 2.29 \times 10^4 \text{ C}$$

$$U_E = \frac{Q^2}{2C} = \frac{1}{2} C \Delta V^2$$

$$U_E = 4 \times 10^9 \text{ Joules.}$$